

# Advel Application Note – AAN2008.3

## Importance of CROWBAR protection on $V_{out}$ of power supplies

Eng. Alessio Spinosi


### 1. Introduction

In switching power supplies, the stabilization function of  $V_{out}$  is usually achieved by the feedback error signal on the oscillator block (PWM).

Now do not care to study the internal circuit in detail, but it's sufficient to say that is used the concept of **feedback**, which can be schematized of using block diagrams, as in Figure 1:

essentially  $V_{out}$  is the stabilized voltage. To keep the output  $V_{out}$  stable it is, through the block **B**, compared with a reference voltage  $V_{ref}$ .

For example, if  $V_{in}$  drops, through block **A** also  $V_{out}$  decreases, but after the difference with the reference voltage, there is a positive signal in the input of block **A**, which offset the decrease in  $V_{in}$ . The reverse occurs if the input voltage tends to increase. As you can see, the system works even if the output voltage changes as a result of the input voltage or due to load variations.

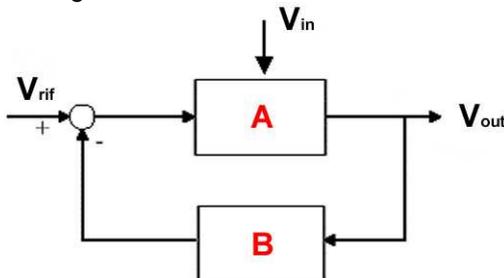

**Figure1** – Block diagram for a feedback system, which can be applied to the control of  $V_{out}$  in a stabilized power supply

The control of  $V_{out}$  is maintained by one or more integrated circuits which perform the "calculations" necessary for stabilization. What you need to ask is:

what happens if one or more parts of the control circuitry of  $V_{out}$  goes in fault?

In case of failure in one or more parts of the control circuitry of  $V_{out}$ , the power supply may behave in different ways, depending on the type of failure or the presence or absence of the protections in the power supply.

### 2. Failure in the control of $V_{out}$

In any system, the worst event that can happen is that a failure in the power supply can damage the loads that it's powering (which often cost much more than the power supply itself).

In any power supply, some failures cause input overload, and the input fuse opens, therefore do

not cause any damage to the load because the power is shut off.


However if the fault occurs on the control of output voltage (**B** block in the block diagram of Figure 1), basically two events can happen:

1.  $V_{out}$  drops than its nominal value;
2.  $V_{out}$  increases compared to its nominal value.

While the first of the two cases is not serious, the second is the absolute worst case: the output voltage rises (typically can reach twice the nominal voltage) and consequently the loads connected to it are damaged.

### 3. Failure in the control of $V_{out}$ in a redundant system

Given a system of power supplies in parallel, what happens if one of them has a fault in the control that causes its  $V_{out}$  to rise?

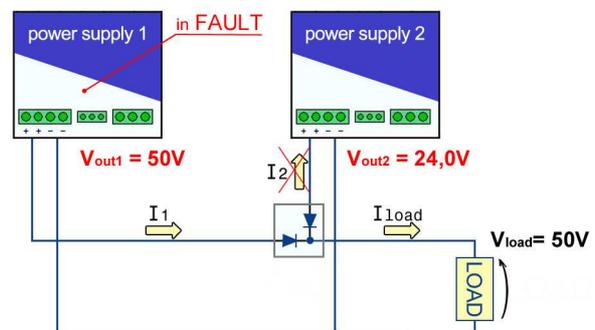

**Figure2** – System of 2 redundant power supplies: one of them was in failure in the  $V_{out}$  control, and  $V_{out}$  rises

Figure 2 shows a system of two power supplies ( $V_{out,nom} = 24V$ ), the first of which was a failure in the control of  $V_{out}$ , that reaches 50V. Well: the load "sees" the 50V, which is the highest voltage between the two voltages in parallel (this is a natural rule, which applies to every type of power supply).


Therefore neither the redundancy can help in case of failure of the control of  $V_{out}$ .

### 4. Protection of $V_{out}$

Many power supplies on the market provide an output overvoltage protection: this is typically a second control circuitry involved in the case of failure of the first control circuitry.

For example, given a power supply,  $V_{out,nom} = 24V$ : in case of failure on the first control of output voltage, the second control intervenes to stabilize  $V_{out}$  at about  $26 \div 27V$ , which is a voltage which certainly does not damage the load.

In this case, continuing the example in Figure 2, if the power supply that goes in fault in the control of  $V_{out}$ , is equipped with the aforesaid overvoltage protection, the situation that would occur is shown in Figure 3.

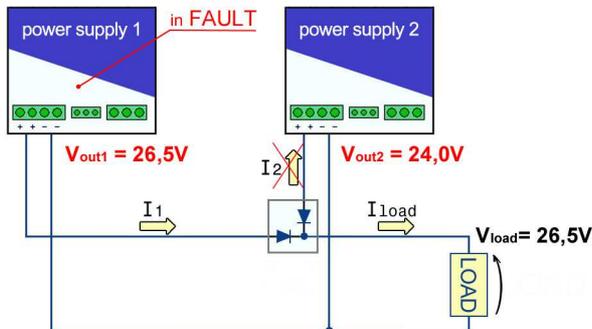

**Figure3** – System of 2 power supplies in redundancy: one has a fault in the control of  $V_{out}$  that cause the increase of  $V_{out}$ , but the power supply is equipped with overvoltage protection on the output.


Well described by the example in Figure 3, we understand how important is the presence of an overvoltage protection on the output, however, present in 70% of industrial power supplies on the market.

Now, there is still a risk that the second control circuit goes in fault or that the failure in the power supply is at the stage of driving the mosfet (block **A** in the block diagram of Figure 1): how you can protect yourself from this possibility, remote but still always possible? It's important prevent this event, especially if the loads they cost a lot.

### 5. CROWBAR protection of $V_{out}$

Advel proposes, as an available option for all range of power supplies (SPS modules for rack or DIN series), in addition to the ever-present standard overvoltage protection, a second protection of  $V_{out}$ , which gives an extra safety that  $V_{out}$  does not exceed a certain value limit: it is a **CROWBAR** protection of output.

This protection is very simple (and so effective): **CROWBAR** the circuitry (which is completely independent of the control circuitry, block **A** and **B** in Figure 1) reads the output voltage  $V_{out}$ , and if it exceeds a certain threshold, a net short circuit in the output is generated (before the parallel-diode, of course).

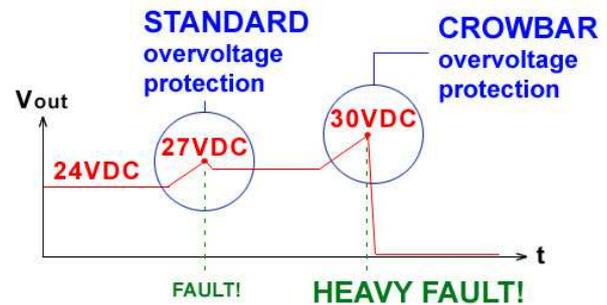

**Figure4** – Example of a standard overvoltage protection intervention, and CROWBAR intervention in an Advel SPS series power supply, output rated 24VDC

Figure 4 outlines the evolution of output voltage ( $V_{out,nom} = 24VDC$ ) for an Advel power supply: in case of failure in the control of  $V_{out}$ , the standard overvoltage protection intervenes, which blocks the output voltage value at  $26 \div 27V$ . In the event of a disaster, in which the first protection is ineffective, the output voltage tends to rise, but once it reaches 30V, the CROWBAR put in short-circuit the output voltage.

### 6. Conclusions

It have been shown the risks involved when there is a fault on the control of  $V_{out}$  of a power supply: the risk is the damage of the load of the power supply.

Many power supplies on the market incorporate a default protection for  $V_{out}$ , commonly known as overvoltage-protection (OP).

It has been shown the CROWBAR protection of  $V_{out}$  proposed by Advel, which intervenes in case of failure or malfunction of the OP itself, and which provides greater protection to the load.

The protection of CROWBAR, optional, is suggested when the cost of the loads is very high.

**»ADVEL«**  
ELETTRONICA INDUSTRIALE

HEADQUARTER: Via Miglioli 13, Segrate 20090 MI (Italy)  
Technical DPT: Eng. A.Spinosi, [tec@advel.it](mailto:tec@advel.it)